

Compensation Design for Peak Current-Mode Buck Converters

Abstract

Peak Current-Mode Controlled Buck Converters are currently very popular and widely adopted in consumer electronics and computer peripheral power management. This application note presents a design procedure for feedback compensation of peak current-mode buck converters, and also introduces the SIMPLIS tool for circuit simulations and the Mathcad mathematical software for quantitative design, and finally provides the verified results by actual measurements.

Contents

1. Open-Loop Analysis of Peak Current Mode Buck Converters	2
2. Compensation Design of Peak Current-Mode Buck Converters	7
3. The Closed-Loop Analysis of Peak Current-Mode Buck Converters	11
4. Conclusion	13
5. References	13

1. Open-Loop Analysis of Peak Current Mode Buck Converters

Peak current-mode control is implemented by an inner current loop, composed of a current sensing circuit, R_i , with a slope compensation (saw-tooth ramp) circuit. The sensed current ramp is summed with the saw-tooth ramp, and then is compared with the output of the error amplifier, V_c . And the result is used to control the ON-time, T_{ON} , of the MOSFET. The circuit diagram is shown in Figure 1.

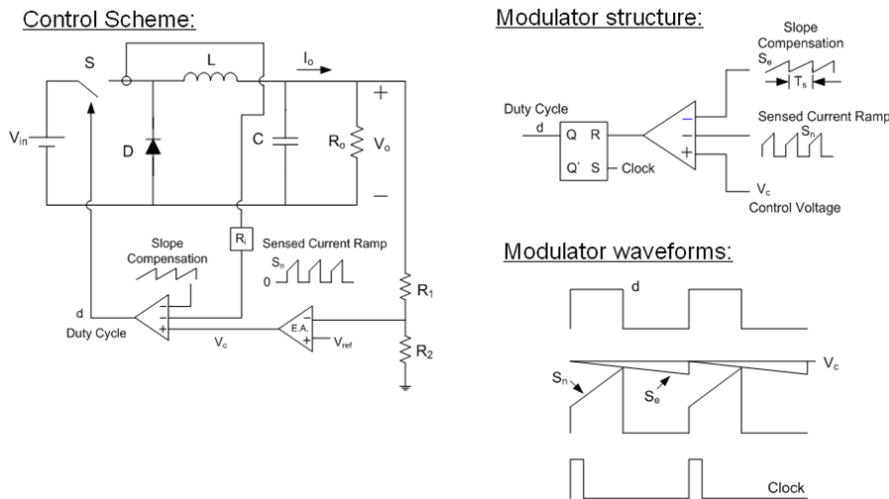


Figure 1. The circuit diagram of a peak current-mode buck converter

For peak current-mode, sub-harmonic oscillation may occur for duty cycle $D > 0.5$. In Figure 2, T_{ON} is the ON-time of the MOSFET, and T_S is the switching period; the dashed line is for the perturbed inductor current, and the solid line is for the ideal steady-state inductor current. For $D < 0.5$, if a perturbation is initiated, it will be completely damped after a few cycles; that is, an unstable state caused by the perturbation will gradually be stabilized. However, for $D > 0.5$, if a perturbation is initiated, it will continue to increase for the next few cycles, which makes the system unstable. Slope compensation is therefore introduced to eliminate the risk of this sub-harmonic oscillation so that the system can remain stable. Slope compensation is implemented by adding a saw-tooth ramp of the same frequency as of the control circuit to the sensed inductor current ramp so that the system can still be stable at duty cycle above 0.5.

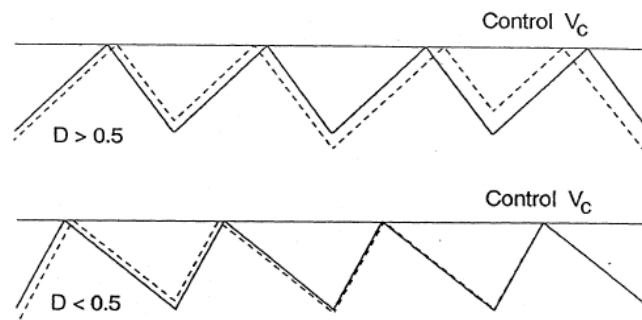


Figure 2. The sensed inductor current ramps by R_i at duty cycles $D < 0.5$ and $D > 0.5$

The small-signal model of a peak current-mode buck converter [1] [2] will be introduced in this section. The Buck PWM Switch Model, proposed by V. Vorperian [1] and the small-signal model for peak current-mode control, by Raymond B. Ridley [2] are displayed in Figure 3. The equations derived according to the model will be applied in compensation design for peak current-mode buck converters.

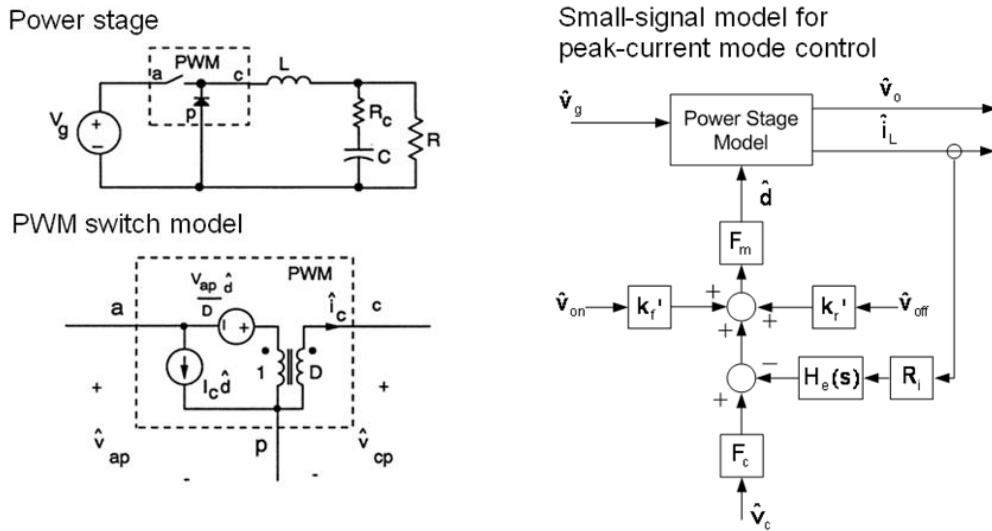


Figure 3. The Buck PWM switch model and the small-signal model for peak current-mode control

The open-loop transfer function of a peak current-mode buck converter is listed below [1], [2]:

$$G_d(s) = \frac{R_o}{R_i} \cdot \frac{1}{1 + \frac{R_o \cdot T_s}{L_1} \cdot [m_c \cdot (1-D) - 0.5]} \cdot F_p(s) \cdot F_h(s) \tag{1}$$

$F_p(s)$ in Equation (1), which dominates the open-loop low-frequency characteristics of this configuration, is shown below, as Equation (2), which has a zero and a pole.

$$F_p(s) = \frac{1 + s \cdot C_{out} \cdot R_C}{1 + \frac{s}{\omega_p}} \tag{2}$$

$F_h(s)$ in Equation (1) represents the high-frequency characteristics of this configuration, where the current-sense transformer R_i plays an important role. $F_h(s)$ is described below, as Equation (3) and it has two high-frequency poles.

$$F_h(s) = \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2} \tag{3}$$

Figure 4 shows a low-frequency dominant pole (at a slope of -20dB / decade), and a high-frequency double pole (at a slope of -40dB / decade decaying). The ESR zero in between is from the ESR of the output capacitor.

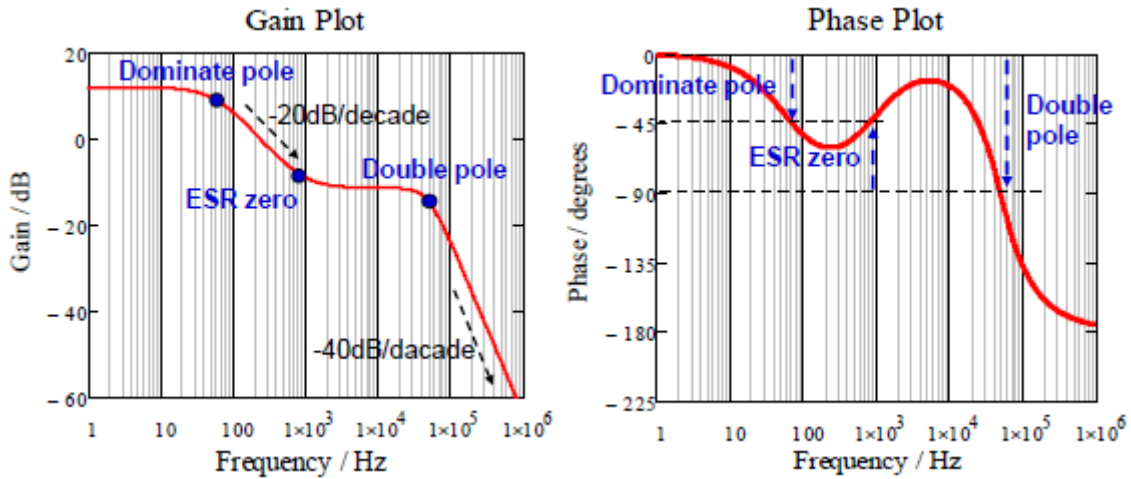


Figure 4. The Bode plot of the open-loop peak current-mode buck converter

The equations for compensation design will be analyzed step by step as follows:

To begin with, the equation of the exact low-frequency pole is presented below:

$$f_{\text{pole}} = \frac{1}{2\pi} \cdot \left[\frac{1}{C_{\text{out}} \cdot R_o} + \frac{T_s}{L_1 \cdot C_{\text{out}}} \cdot [m_c \cdot (1-D) - 0.5] \right] \quad (4)$$

Advanced computational tools will be needed to calculate for the above equation. However, the simplified equation, listed below, is a close approximation, by which the pole can be found quickly.

$$f_{\text{p_approx}} = \frac{1}{2\pi \cdot R_o \cdot C_{\text{out}}} \quad (5)$$

The equation below is for the output capacitor zero


$$f_{\text{zero}} = \frac{1}{2\pi \cdot R_c \cdot C_{\text{out}}} \quad (6)$$

The following equation is for the double pole, positioned at the half of the switching frequency:

$$f_n = \frac{f_s}{2} \quad (7)$$

With the equations above, a design example will be offered to describe the important characteristics of a peak current-mode buck converter.

Figure 5 displayed the circuit diagram and the corresponding circuit parameters of a buck converter. The input voltage is 12Vdc, the rated output current 3A, the output voltage 3.3V, the operating frequency 340kHz, the inductance 10μH, the output capacitance 44μF, and its ESR 5mΩ.

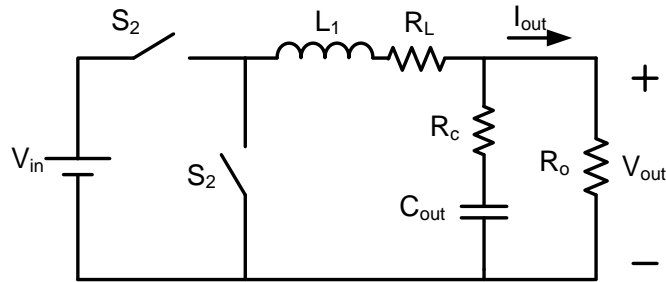

Specifications	Parameters
Input voltage $V_{in} = 12\text{ V}$	Inductance $L_1 = 10\ \mu\text{H}$
Output current $I_{out} = 3\text{ A}$	Inductor DCR $R_L = 10\ \text{m}\Omega$
Output voltage $V_{out} = 3.3\text{ V}$	Output Capacitance $C_{out} = 44\ \mu\text{F}$
Switching frequency $f_s = 340\ \text{kHz}$	Capacitor ESR $R_c = 5\ \text{m}\Omega$

Figure 5. The circuit diagram and the corresponding circuit parameters of a peak current-mode buck converter.

Substitute the above parameters to Equation (4) to obtain a more accurate low-frequency first-order pole, which is located at 4.3kHz.

$$f_{\text{pole}} = \frac{1}{2\pi} \cdot \left[\frac{1}{C_{out} \cdot R_o} + \frac{T_s}{L_1 \cdot C_{out}} \cdot [m_c \cdot (1-D) - 0.5] \right] = 4.322 \times 10^3$$

Slope compensation factor, m_c , is defined as $m_c = 1 + \frac{S_e}{S_n}$, where S_e is the slope of the added compensation saw-tooth ramp and S_n the slope of the sensed current ramp when the switch is on.

$$S_e = \frac{507 \times 10^{-3}}{T_s}, T_s = \frac{1}{f_s}, S_n = \frac{V_{in} - V_{out}}{L_1} \times R_i, R_i = \frac{1}{5.2} = 192\text{m}$$

By Equation (5), the first-order pole, 3.3kHz, can be readily calculated as below.

$$f_{p_approx} = \frac{1}{2\pi \cdot R_o \cdot C_{out}} = 3.288 \times 10^3$$

Substitute the above parameters to Equation (6), and the exact location of the output capacitor ESR zero can be found as 723kHz.

$$f_{\text{zero}} = \frac{1}{2\pi \cdot R_C \cdot C_{\text{out}}} = 723.432 \times 10^3$$

Then, by Equation (7), the high-frequency double pole is obtained as 170kHz.

$$f_n = \frac{f_s}{2} = 170 \times 10^3$$

With all the parameters above plugged in, a Bode plot can be drawn by Mathcad as below. In Figure 6, it can be seen that a pole occurs at low frequency (3.28kHz), and ESR zero (723kHz) occurs at an even higher frequency than the double pole, since the smaller ESR is used.

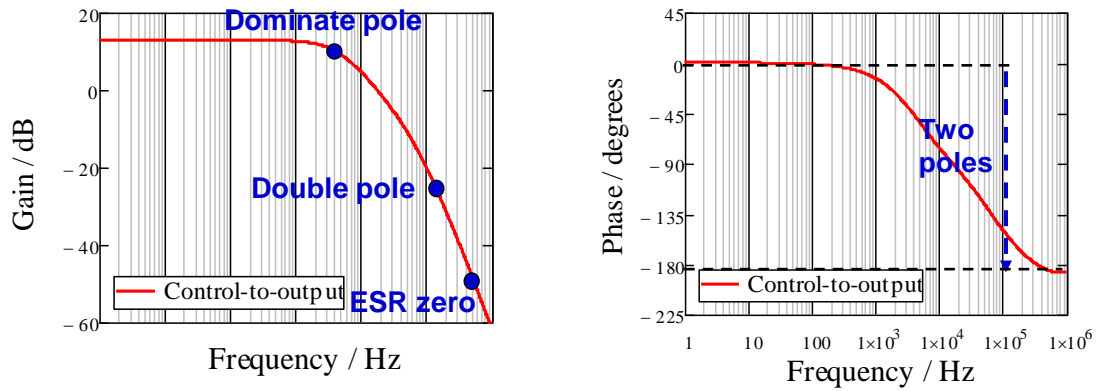


Figure 6. The Bode plot of the open-loop peak current-mode buck converter in the design example

2. Compensation Design of Peak Current-Mode Buck Converters

The previous section has described the characteristics of a peak current-mode buck. In this section, how to compensate peak current-mode buck converters for system stability will be investigated. In Figure 7, the open-loop gain is plotted in red; at low frequencies, the DC gain is low. Low DC gain at low frequencies can cause steady-state errors, which can be seen in Figure 10, for which the frequency responses of two different DC gains with the same bandwidth and phase margin are displayed in Figure 9. For $f > f_c$, the gain curve is at the slope of -40dB/decade , and the phase curve is at the slope of $-90^\circ/\text{decade}$, which often results in insufficient phase margin, illustrated in Figure 8, which furthermore causes system instability. The optimal closed-loop gain is drawn in blue. Compared with the open-loop gain, the closed-loop gain manifests the following advantages: higher DC gain at low frequency so that the steady-state errors can be minimized as in Figure 10, and for $f > f_c$, the gain is at the slope of -20dB/decade , and the phase $-45^\circ/\text{decade}$, as shown in Figure 7, thereby to improve the phase margin (P.M.).

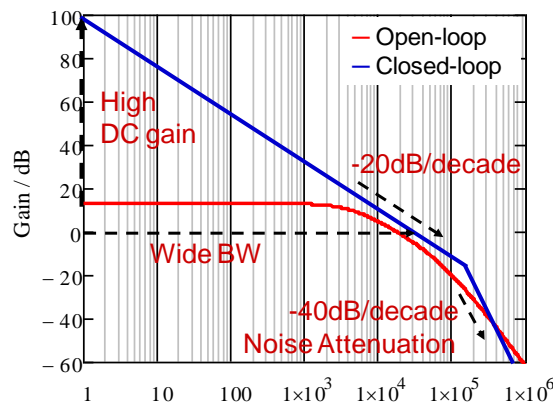


Figure 7. The comparison of the open-loop and closed-loop Bode plots

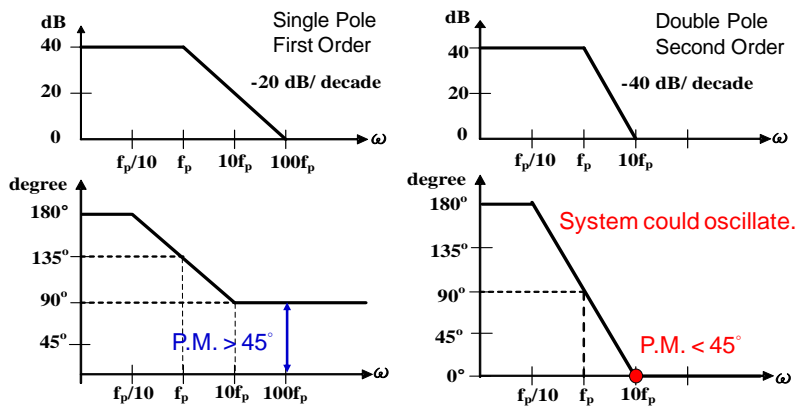


Figure 8. Single pole vs. double pole

Effect of DC Gain

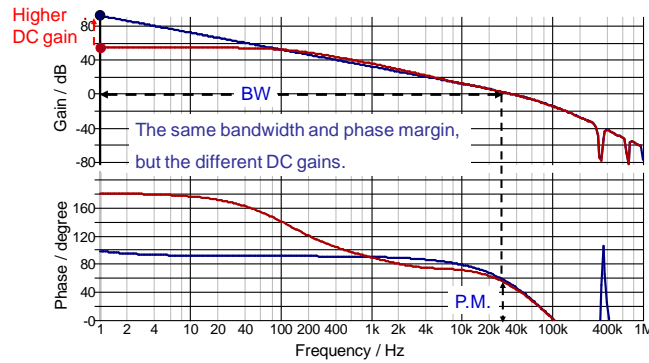


Figure 9. Different DC gains with the same bandwidth and phase margin

In Figure 10, it can be seen load regulation is better with higher DC gain, and worse with lower DC gain.

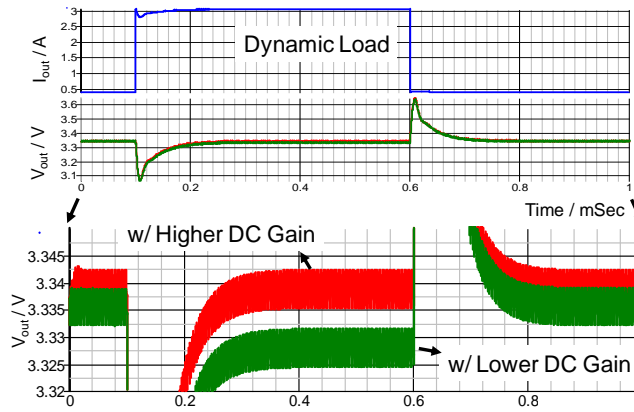


Figure 10. The effect of DC gains on load regulation

Based on the above analysis of the circuit parameters on system performance, what is needed for a compensator is a zero to cancel the low-frequency pole of a peak current-mode buck converter, as in Figure 11, so that the gain curve will be at the slope of -20dB / decade at the crossover frequency, thereby to achieve a better phase margin. At high frequencies, a high-frequency compensator pole can help filter out high-frequency noises.

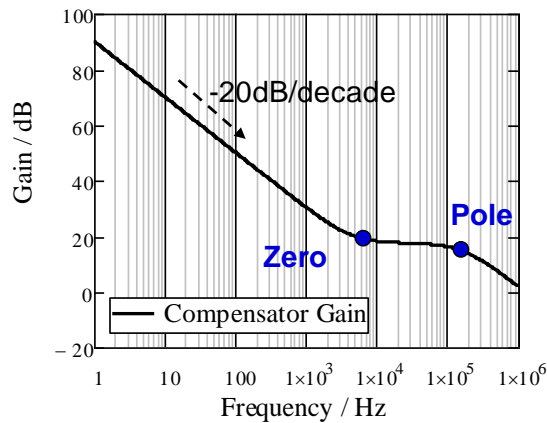


Figure 11. A compensator offers a zero and a pole

Take a GM-Type compensator below as an example. Since a GM-Type compensator has one zero and two poles, it is quite suitable to compensate peak current-mode buck converters. First pole can be obtained from R_{gm} and C_{comp} , the other pole from R_{comp} and C_{gm} , and a zero from R_{comp} and C_{comp} .

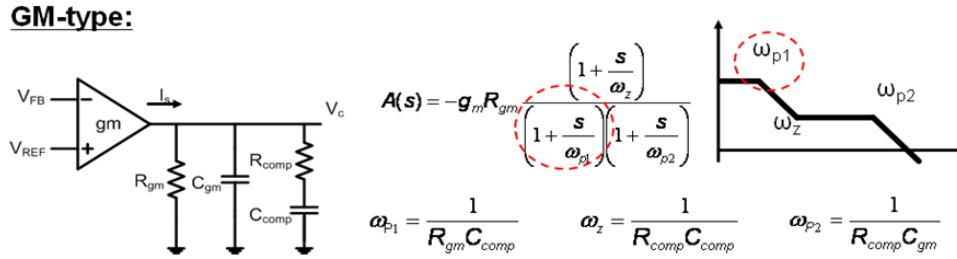


Figure 12. A GM-Type compensator

Compensator Design Procedure :

Step 1 :

Set the crossover frequency (i.e. the bandwidth). In the example above, the operating frequency is 340kHz, and the bandwidth is usually set as 1/10 of the operating frequency.

$$f_c = 34 \times 10^3 \tag{8}$$

Step 2 :

Set the zero of the compensator to cancel the pole of the peak current-mode buck topology.

$$f_z = f_{pole} = 4.322 \times 10^3 \tag{9}$$

Step 3 :

The compensator pole is set to the lower frequency among the ESR zero and 1/2 of the operating frequency. In this example, 1/2 of the operating frequency is lower than the ESR zero, so set the compensator pole to 1/2 of the operating frequency.

$$f_p = \frac{1}{2} \cdot f_s = 170 \times 10^3 \tag{10}$$

Step 4 :

By Mathcad, the phase margin of 48° can be obtained by the following equation. Usually for stability, the phase margin should be greater than 45°.

$$\Phi_M = \Phi_{fc} + 180 - 90 + \text{atan}\left(\frac{f_c}{f_z}\right) \cdot \frac{180}{\pi} - \text{atan}\left(\frac{f_c}{f_p}\right) \cdot \frac{180}{\pi} = 48.918 \tag{11}$$

Step 5 :

From Equation (12), the DC gain, increased by the compensator at the crossover frequency, can be calculated as 17.4dB.

$$G_A = -G_{fc} - 20 \cdot \log\left(\frac{V_{REF}}{V_{out}}\right) + 20 \cdot \log\left(\text{ceil}\left(\frac{f_c}{f_p}\right)\right) - 20 \cdot \log\left(\text{ceil}\left(\frac{f_z}{f_c}\right)\right) = 17.371 \quad (12)$$

Step 6 :

The parameters of the compensator in this example, such as $R_{comp} = 5.9k\Omega$, $C_{comp} = 6.23nF$, $C_{gm} = 158pF$, can all be obtained as follows.


$$g_m = 1.25 \times 10^{-3}$$

$$R_{gm} = 200 \times 10^6$$

$$R_{comp} = 10^{\frac{G_A}{20}} \cdot \frac{1}{g_m} = 5.911 \times 10^3$$

$$C_{comp} = \frac{1}{2\pi \cdot f_z \cdot R_{comp}} = 6.23 \times 10^{-9}$$
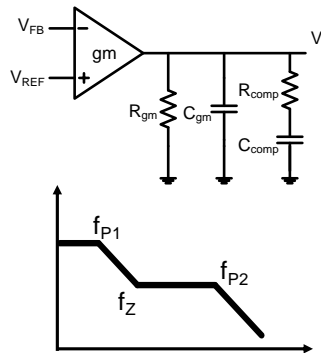
$$C_{gm} = \frac{1}{2\pi \cdot f_p \cdot R_{comp}} = 158.393 \times 10^{-12}$$



Step 7 :

Substitute all the above numbers into Equation (13), then enter the equation into Mathcad, and the Bode plot of the compensator can be drawn, seen in Figure 13.

$$\omega_{p1} = \frac{1}{R_{gm} \cdot C_{comp}} \quad \frac{\omega_{p1}}{2\pi} = 127.741 \times 10^{-3}$$

$$\omega_z = \frac{1}{R_{comp} \cdot C_{comp}} \quad \frac{\omega_z}{2\pi} = 4.322 \times 10^3$$

$$\omega_{p2} = \frac{1}{R_{comp} \cdot C_{gm}} \quad \frac{\omega_{p2}}{2\pi} = 170 \times 10^3$$

$$A = -g_m \cdot R_{gm} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \cdot \left(1 + \frac{s}{\omega_{p2}}\right)} \quad (13)$$

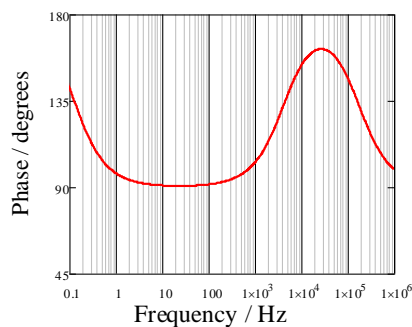
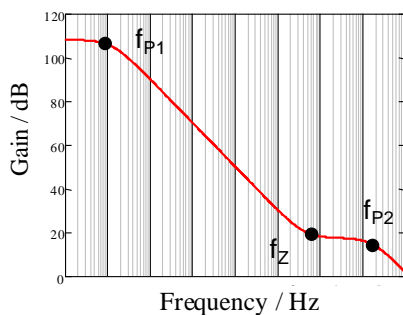


Figure 13. The Bode plot of the compensator

3. The Closed-Loop Analysis of Peak Current-Mode Buck Converters

In this section, the SIMPLIS tool is used to simulate the peak current-mode buck converter and to substantiate the closed-loop frequency response analysis. The SIMPLIS schematic is displayed in Figure 14. The closed loop of this current-mode buck converter incorporates a current sensor, a compensator, and a slope compensation circuit.

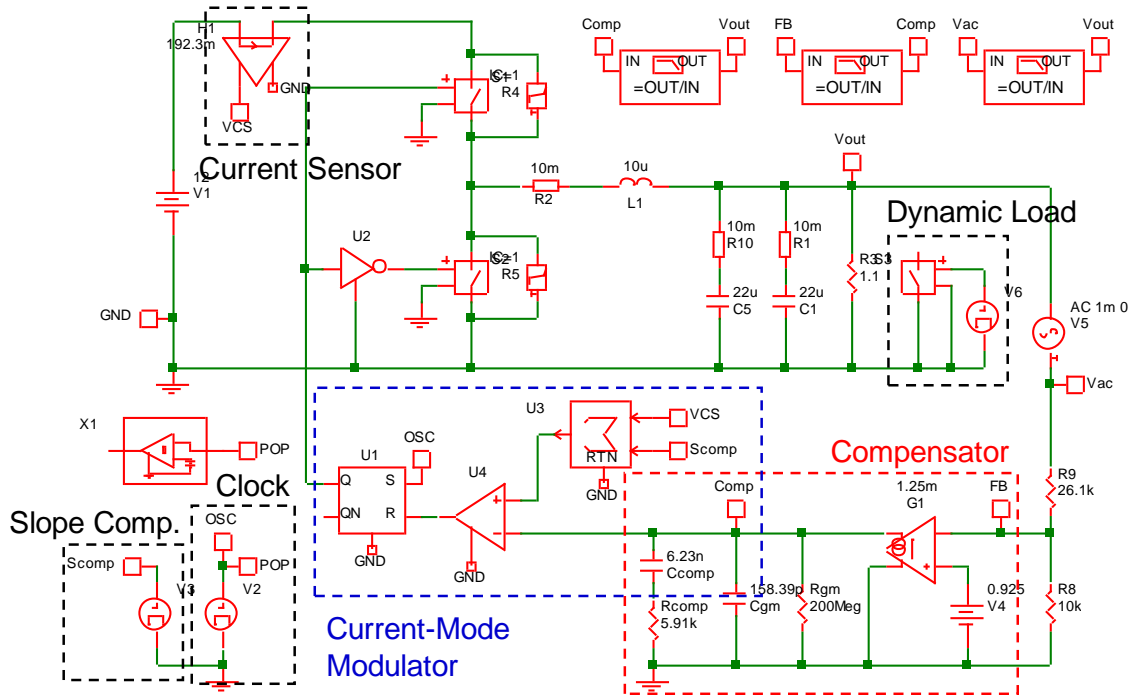


Figure 14. The SIMPLIS simulation schematic (the closed-loop peak current-mode buck converter)

In Figure 15, the equation from the previous section (red line) is drawn by Mathcad, which is verified with the simulation result (blue dots) of the SIMPLIS schematic in Figure 14. It demonstrates that the simulation result closely aligns with the analytical result, derived by Mathcad, and the bandwidth and phase margin are 34kHz and 48.9°, respectively.

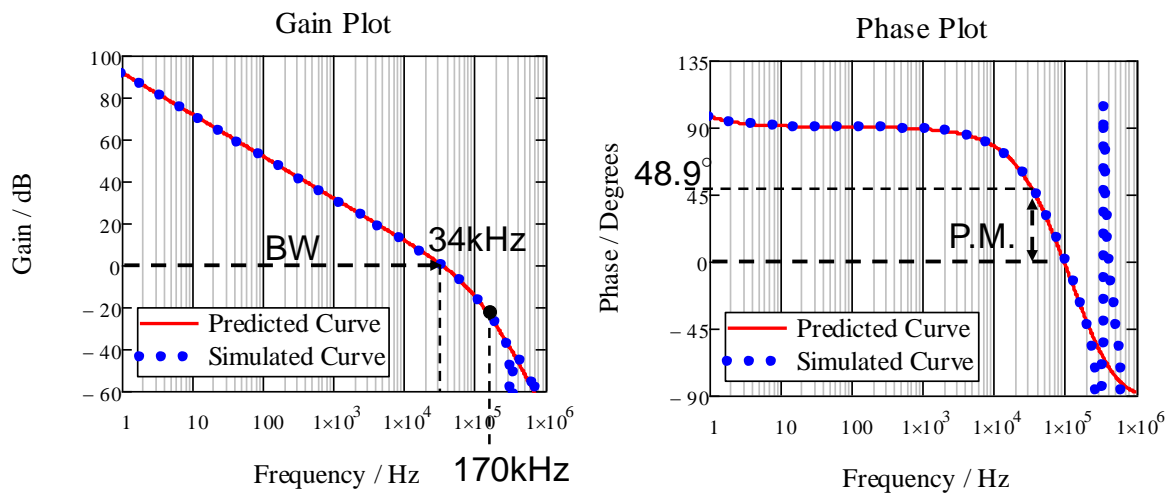


Figure 15. The comparison of theoretical analysis with the Matchcad and the SIMPLIS simulation

Figure 16 has exhibited the benefits a compensator can provide. First, a compensator (black dashed line) enhances DC gain in the low frequency range. The open loop response (red line), combined with the compensator response (black dashed line), makes the closed loop response (blue line). Second, a compensator increases bandwidth, as in Figure 16, the crossover frequency in blue is greater than that in red. Third, a compensator adds one high-frequency pole, which improves high-frequency noise immunity (at high frequency, the blue line drops faster than the red line). Fourth, the zero of a compensator helps achieve a sufficient phase margin.

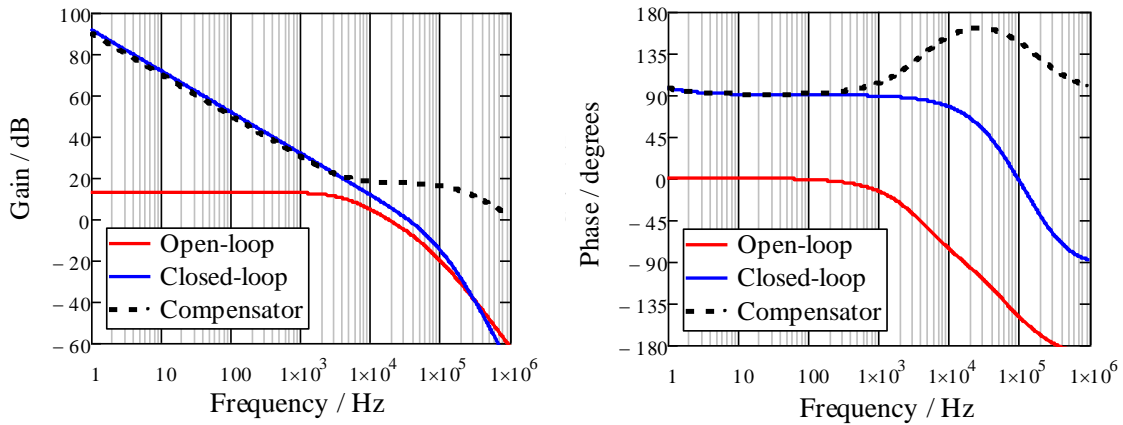


Figure 16. The comparison between the open loop and the closed loop

An actual measurement setup is presented in Figure 17, and an AC perturbation signal is injected into point R. The gain and phase plot can be obtained by measuring the output (point A) versus the input (point R). From the right-hand plot of Figure 17, the measured result (green line) shows good agreement with the analytical result (red line).

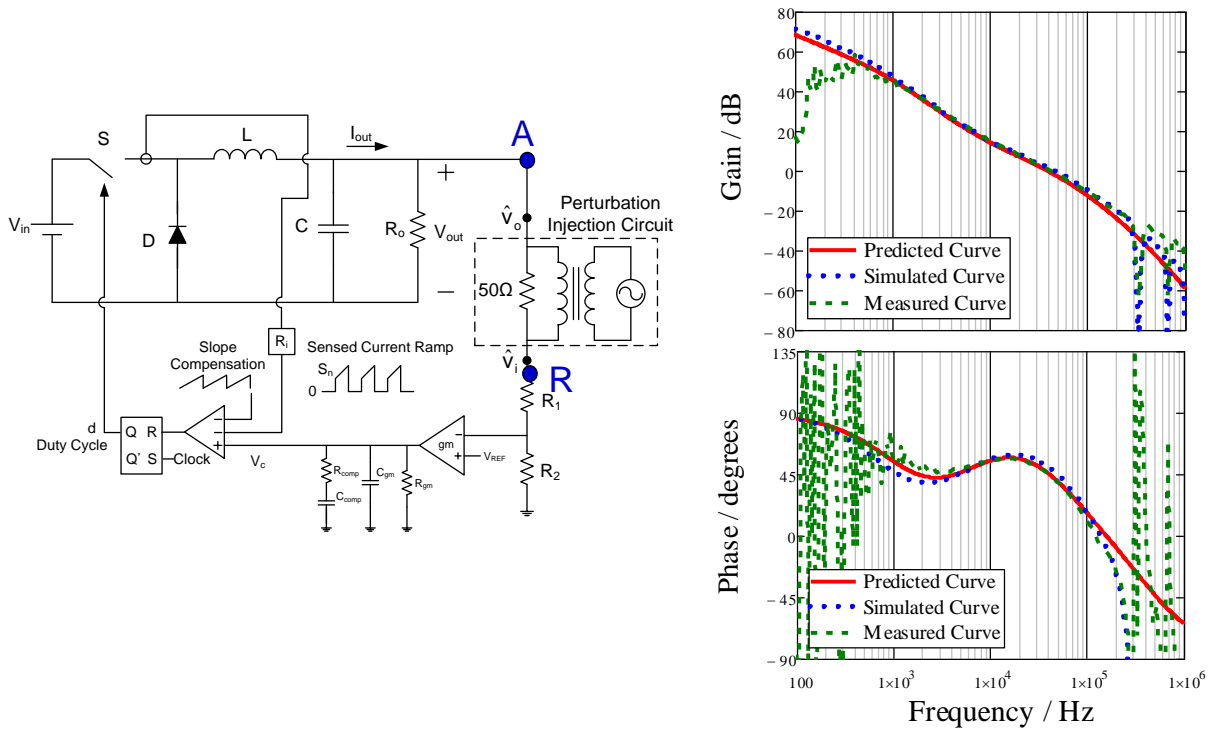


Figure 17. The experimental results verify the closed loop frequency response

4. Conclusion

- At low frequencies, an open-loop peak current-mode buck converter is still a single-pole system since the loop control is realized by injecting current signals into the loop only.
- Its compensator is easy to design. The compensator zero is designed to cancel the dominant pole of a buck converter for system stability.
- In order to assure sufficient phase margin, the design goal is that the gain curve is at the slope -20dB / decade, when passing the crossover frequency.

5. References

- [1] V. Vorperian, "Simplified analysis of PWM converters using model of PWM switch part I: continuous conduction mode," IEEE Trans. on Power Electronics, vol. 26, no. 3, pp. 490-496, May 1990.
- [2] Raymond B. Ridley, A New Small-signal Model for Current-mode Control, Ph.D. Dissertation, Virginia Polytechnic Institute and State University, Nov. 1990.

Next Steps

Richtek Newsletter

[Subscribe Richtek Newsletter](#)

Richtek Technology Corporation

14F, No. 8, Tai Yuen 1st Street, Chupei City
 Hsinchu, Taiwan, R.O.C.
 Tel: 886-3-5526789

Richtek products are sold by description only. Richtek reserves the right to change the circuitry and/or specifications without notice at any time. Customers should obtain the latest relevant information and data sheets before placing orders and should verify that such information is current and complete. Richtek cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Richtek product. Information furnished by Richtek is believed to be accurate and reliable. However, no responsibility is assumed by Richtek or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Richtek or its subsidiaries.